

## **Combinatorial Logic**

Submitted by

Caleb Burke

658780838

Department of Computer Science

Faculty of Science and Technology

Vancouver Island University

## **CSCI 355 Digital Logic and Computer Organization**

Submitted to

Prof. Ajay Shrestha

September 24, 2024

## Table of Contents

### Contents

1. Objectives.....	1
2. Components Required.....	1
3. Background (You can remove this section).....	1
4. Pre-Lab.....	2
6. Lab Procedure with Deliverables.....	3
7. Conclusion.....	6
References.....	6
Appendix.....	6

## **1. Objectives**

1. Design multibit adder using Verilog HDL
2. Design multibit comparator using Verilog HDL
3. Interpret waveforms generated with input/output signals

## **2. Components Required**

Power supply, 1 x 7400 Quad 2-Input NAND Gate, 1 x 7402 Quad 2-Input NOR Gate, Breadboard, Digital Circuit Evaluator, Wiring Kit

## **4. Pre-Lab**

**4.1 Why is a multi-bit adder processed from the least-significant bit to the mostsignificant bit while a multi-bit comparator is processed from the mostsignificant bit to the least-significant bit?**

**4.2 Write the decimal number 7129 in different representationsin Verilog HDL:**

Binary = ?

Octal = ?

Hex = ?

Decimal =

## 6. Lab Procedure

### 6.1 N-bit adder

#### 1. fulladder

Verilog main code and testbench code attached.



Timing diagram

## 2. Eight bit adder


Verilog main code and testbench code attached.



Timing diagram
 
### 3. 32 bit adder

Verilog main code and testbench code attached.




Timing diagram

## 6.2 Four bit comparator
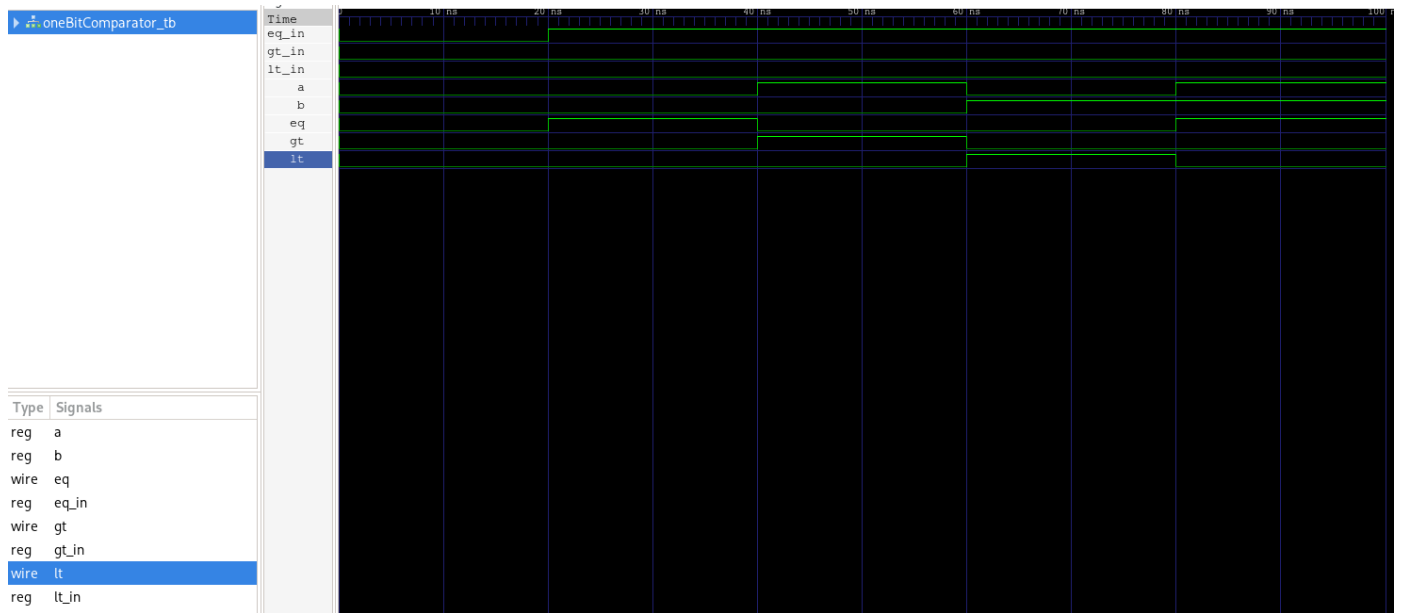
### 1. One bit comparator


Verilog main code and testbench code attached.



Timing diagram
 
## 2. Four bit comparator

Verilog main code and testbench code attached.



## Timing diagram

## 7. Conclusion

In this lab, I implemented and tested a multi-bit adder and comparator using Verilog HDL. Time diagrams confirmed functionality and reinforced core concepts.

## Appendix

Signature: Caleb Burke