

## **Combinatorial Logic**

Submitted by

Caleb Burke

658780838

Department of Computer Science

Faculty of Science and Technology

Vancouver Island University

## **CSCI 355 Digital Logic and Computer Organization**

Submitted to

Prof. Ajay Shrestha

September 24, 2024

## Table of Contents

### Contents

1. Objectives.....	1
2. Components Required.....	1
3. Background (You can remove this section).....	1
4. Pre-Lab.....	2
6. Lab Procedure with Deliverables.....	3
7. Conclusion.....	6
References.....	6
Appendix.....	6

**1. Objectives**

- I. Familiarization with Full Adder
- II. Familiarization with Parity Generator and Checker
- III. Construct Full-Adder using NAND and XOR only logics
- IV. Construct NAND equivalent for combinational circuit
- V. Construct NOR equivalent for combinational circuit

**2. Components Required**

Power supply, 7400 Quad 2-Input NAND Gate, 7402 Quad 2-Input NOR Gate, 7486 Quad 2- input XOR, Breadboard, Digital Circuit Evaluator, Wiring Kit

**4. Pre-Lab****4.1 Boolean Function**

4.1.1 Use algebraic manipulation to prove

I.  $x + yz = (x + y) * (x + z)$

$$\begin{aligned}
 x + yz &= (x + y)(x + z) \\
 &= x(x + y) + z(x + y) \\
 &= xx + xy + xz + yz \\
 &= x + xy + xz + yz \text{ (absorption)} \\
 &= x + xz + yz \text{ (absorption)} \\
 &= x + yz
 \end{aligned}$$

ii.  $xy + yz + !xz = xy + !xz$

$$\begin{aligned}
 xy + yz + !xz &= xy + !xz \\
 xy + !xz &= xy + !xz \text{ (absorption)}
 \end{aligned}$$

$$\text{iii. } !(((a + b) + !c + !d) * !(ab) * !c * !d)) = !(a + b) * c * d + a * b + c + d$$

$$!(((a + b) + !c + !d) * !(ab) * !c * !d)) = !(a + b) * cd + ab + c + d$$

RHS

$$!(a + b) * cd + ab + c + d$$

LHS

$$!((a + c) + (!c + !d)) + !(ab) * !c * !d$$

$$!(a + b) * !(c + !d) + !(ab) + !c + !d$$

$$!(a + b) * c * d + ab + c + d$$

$$\text{LHS} == \text{RHS}$$

4.1.2 Use algebraic manipulation to find the minimum sum-of-products (SOP) expression for the function:

$$\text{let } a = x_1, b = x_2, c = x_3, d = x_4$$

$$\begin{aligned} f &= a * !b * !c + abd + a * !b * c * !d \\ &= a(!b!c + bd + !bc!d) \\ &= a(!b!c + !bc!d + bd) \\ &= a(!b(!c + c!d) + bd) \\ &= a(!b(!c + !d) + bd) \end{aligned}$$

i.e

$$x_1 \& (((!x_2) \& ((!x_3) | (!x_4)))) | (x_2 \& x_4))$$

$$\begin{aligned}
f(x_1, x_2, x_3) &= \text{sum} ( m(1, 3, 4, 6, 7) ) \\
&= (!x_1 * !x_2 * x_3) + (!x_1 * x_2 * x_3) + (x_1 * !x_2 * !x_3) + (x_1 * x_2 * !x_3) + (x_1 * x_2 * x_3) \\
&= (!x_1 * !x_2 * x_3) + (!x_1 * x_2 * x_3) + (x_1 * !x_2 * !x_3) + (x_1 * x_2) \\
&= (!x_1 * x_3) + (x_1 * !x_2 * !x_3) + (x_1 * x_2) \\
&= (!x_1 * x_3) + x_1 * (!x_2 * !x_3 + x_2) \\
&= !x_1 * x_3 + x_1 * (x_2 + !x_3)
\end{aligned}$$

4.1.3 Use algebraic manipulation to find the simplest products-of-sums (POS) circuit that implements the function:

$$\begin{aligned}
f(x_1, x_2, x_3) &= \text{mul} ( M(0, 2, 5) ) \\
&= (!x_1 + !x_2 + !x_3) * (!x_1 + x_2 + !x_3) * (x_1 + !x_2 + x_3) \\
&= (!x_2 + (!x_1 + !x_3)) * (x_2 + (!x_1 + !x_3)) * (x_1 + !x_2 + x_3) \\
&= (!x_1 + !x_3) * (x_1 + !x_2 + x_3)
\end{aligned}$$

## 4.1.4 Find the minimum-cost SOP and POS forms for the function

$$f(x_1, x_2, x_3) = \text{sum} ( m(1, 2, 3, 5) )$$

SOP

$$m(1) = \neg x_1 * \neg x_2 * x_3$$

$$m(2) = \neg x_1 * x_2 * \neg x_3$$

$$m(3) = \neg x_1 * x_2 * x_3$$

$$m(5) = x_1 * \neg x_2 * x_3$$

	x <sub>2</sub> /x <sub>3</sub>			
x <sub>1</sub>	00	01	11	10
0	0	1	1	1
1	0	1	0	0

$$f(x_1, x_2, x_3) = \neg x_2 * x_3 + \neg x_1 * x_2$$

POS

$$M(0) = x_1 + x_2 + x_3$$

$$M(4) = \neg x_1 + x_2 + x_3$$

$$M(6) = \neg x_1 + \neg x_2 + x_3$$


$$M(7) = \neg x_1 + \neg x_2 + \neg x_3$$

	x <sub>2</sub> /x <sub>3</sub>			
x <sub>1</sub>	00	01	11	10
0	1	0	1	1
1	0	0	1	0

$$f(x_1, x_2, x_3) = (x_1 + \neg x_2) * (\neg x_2 + x_3) * (x_1 + x_2 + \neg x_3)$$

## 4.2 Full Adder Implementation

Just NAND and XOR

 


## 4.3 Parity Generator

The circuit shown in 7.2 tells if the 5 input bits are an odd number of 1's. Return of 1 is odd, return of 0 is even. Parity bit is for error detection; if the number of 1's is even but parity is 1, some error has occurred. This integrity check works even if the parity bit itself is corrupted. Note that the parity bit only gives us info that some data corruption has occurred.

## 7. Lab Procedure with Deliverables

### 7.1 Full adder

Picture of circuit

 




Truth Table

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## 7.2 Parity Generator

Picture of circuit

 

Truth Table

A0	A1	A2	A3	A4	X
0	0	0	0	0	0
0	0	0	0	1	1
0	0	0	1	0	1
0	0	0	1	1	0
0	0	1	0	0	1
0	0	1	0	1	0
0	0	1	1	0	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	0	1	0
0	1	0	1	0	0
0	1	0	1	1	1
0	1	1	0	0	0
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	0	1	1

1	0	1	1	0	1
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	0	1	1
1	1	0	1	0	1
1	1	0	1	1	0
1	1	1	0	0	1
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	1

## Appendixs

Signature: Caleb Burke